

Candidate No: _____

KADI SARVA VISWAVIDHYALAYA

MCA – Semester I (ATKT)

MC 02 – Fundamentals of Computer Organization

Date: 09-04-2013

Time: 10.00am – 1.00pm

Total Marks: 50

Instructions

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Q1. Answer the following

[10]

- a) Convert the binary number 111011.1011 to its equivalent decimal representation.
- b) Convert the decimal number 632.97 to its equivalent octal representation.
- c) Perform binary multiplication on $10111.1 * 1011.11$
- d) Perform 2's complement on -42-20
- e) Perform 10's complement on 24 -68

Q2(a). Fill up the following.

[10]

- 1) Excess-3 code is also known as _____.
- 2) _____ is a means to describe how the output of a logic circuit depends on the logic level present at the input.
- 3) A logic circuit that adds three 1-bit number is called as _____.
- 4) A group of _____ stores more than 1 bit of digital data.
- 5) The data stored in memory in terms of groups of binary bits are called as _____.

Q2(b). 1) What is 2-4-2-1 code?

2) Minimize the following expression using K-Map

$$Y(A,B,C,D) = \sum m(0,2,4,7,8,10,12,13)$$

(Or)

1) State DeMorgan's Theorems

2) Minimize the following expression using K-Map

$$Y(A,B,C,D) = \prod M(1,2,3,8,9,10,11,14) \cdot d(7,15)$$

Q3. Answer the following

[10]

- a) List out the steps to design a combinational logic circuit using gates and design a 1 bit comparator using logic gates.
- b) Explain in detail about Full Adder.

(Or)

P.T.O

- a) Write the algorithm of 9's complement BCD subtraction and explain it with an example.
- b) What are the applications of multiplexer? Implement the following expressions using a multiplexer. $Y(A,B,C) = \prod M(0,1,4,5)$

Q4. Answer the following

[10]

- a) What is the limitation of S-R flip flop? How is it rectified in J-K flip flop? Explain them.
- b) State any 5 characteristics of flip-flops.

(Or)

- a) Explain the excitation table of RS and JK flip flops.
- b) Explain in detail about asynchronous loading of PISO shift register.

Q5. Answer the following

[10]

- a) Draw the functional diagram of the memory and explain its components.
- b) Briefly explain about any 5 characteristics of memory.

(Or)

- a) What are interrupts? Explain its types.
 - b) Explain Instruction Cycle.
-