

**L.D.R.P Institute of Technology and Research, Gandhinagar**  
**Electronics & Communication Engineering Department**  
**KSV Mid-Semester Examination -2015**

**Subject Name:** Advance Electronics

**Date:**02/03/2015

**Subject Code:** EC-403

**Time:**12:30 to 1:30pm

**Semester:** 4<sup>th</sup>

**Total Marks:** 30

- 
- Instructions:** 1. Attempt all questions.  
2. Make suitable assumptions wherever necessary.  
3. Figures to the right indicate full marks.
- 

- Q.1 Define Oscillator. What are the requirement of positive feedback amplifier as an oscillator & also explain Barkhausen criterion of oscillations. (08)
- Q.2 A) Write and Explain Difference between positive feedback and negative feedback (06)
- B) Define Amplifier & make a comparison table of Different amplifier with their classes. (06)

**OR**

- Q.2 A) Determine the voltage gain, input and output impedance with feedback for voltage series feedback having (06)

$A = -100$ ,  $R_i = 10\text{ K}\Omega$ ,  $R_o = 20\text{ K}\Omega$  for feedback of

- a)  $\beta = -0.1$  and
- b)  $\beta = -0.5$
- B) Make short note on Amplifier Distortion. Also make graphical description of Harmonic components of distorted signal. (06)

- Q.3 Write down the Limitation of RC and LC oscillators. explain characteristic of crystal and base on that explain transistor crystal oscillator. (10)

Calculate, if  $L = 800\text{ mH}$ ,  $C = 0.01\text{ pF}$ ,  $R = 1000\text{ }\Omega$  and  $C_m = 20\text{ pF}$  are the Various Value of an ac equivalent circuit of a piezoelectric crystal. Determine  $f_s$  and  $f_p$  of the crystal.

**OR**

- Q.3 A) Design and explain R-2R ladder DAC when digital input is 100. (05)
- B) Write Shot Note On Successive- Approximation ADC. (05)

**All the Best**