

KADI SARVA VISHWAVIDYALAYA

B.E SEMESTER IV EXAMINATION (MAY/2014)

SUBJECT CODE : EC- 403

SUBJECT NAME : ADVANCE ELECTRONICS

DATE: 13/05/2014

TIME: 10:30 TO 1:30

TOTAL MARKS: 70

Instructions:

1. Answer each section in separate Answer Sheet.
2. Use of scientific Calculator is permitted.
3. All questions are compulsory.
4. Indicate **clearly**, the options you attempted along with its respective question number
5. Use the last page of main supplementary for rough work.

Section - 1

Q:1 (All Compulsory)

- (A) Explain the Switched mode power supply (SMPS) with necessary diagram. 05
- (B) Explain class B push pull amplifier. 05
- (C) Classify the amplifiers based on position of operation point (Q - Point) and also explain the Distortion in amplifier. 05

OR

- (C) Draw and Explain a simplified circuit diagram of a regulated power supply and what type Of feedback is employed by this regulator? 05

Q:2 Answer the following Question.

- (A) Explain the UJT as a Relaxation Oscillator. 05
- (B) Write short note on mono stable multivibrator. 05

OR

- (A) Explain construction, working and characteristic of UJT. 05
- (B) Explain construction and working of Tunnel diode. 05

Q:3 Answer the following Question.

- (A) Explain the advantages and disadvantages of negative feedback. 05
- (B) What are the four possible topologies of feedback amplifier? Draw any two with necessary Details showing V_i , V_o , R_i , R_o , I_i , and I_o . Derive input and output resistance for any one Topology. 05

OR

- (A) Calculate A_{vf} , R_{of} and R_{if} for an amplifier with voltage series feedback. Assume $R_s=0$, $h_{fe}=50$, $h_{ie}=1.1K$, $h_{re}=h_{oe}=0$, $R_e=4.7K$. 05
- (B) Obtain G_{Mf} , A_{Vf} , and R_{if} expressions for single stage BJT-based current series feedback amplifier. Draw necessary circuit schematics. 05

Section - 2

Q:4 (All Compulsory)

- (A) Draw the hybrid π model for a transistor in CE configurations and explain it. Derive the equation for transconductance g_m . 05
- (B) Explain working principal of colpitt's oscillator. Also derive the expression for frequency of Oscillations. 05
- (C) Design RC phase shift oscillator for the frequency of 10 kHz. 05

OR

(C) Write short note on: Validity of Hybrid – PI model. 05

Q:5 Answer the following Question.

- (A) State and explain any five characteristics of an ideal Op-Amp. 05
- (B) Draw and explain the block diagram of an Op-Amp. 05

OR

- (A) Derive the expression of voltage gain for inverting and non inverting mode of an OP-AMP. 05
- (B) Show the circuit and explain how to measure Input Bias Current and CMRR of an OP-AMP. 05

Q:6 Answer the following Question.

- (A) Draw 4-bit R-2R ladder type DAC and explain its working. 05
- (B) Explain working of successive approximation ADC with block diagram. 05

OR

- (A) Explain Dual slope A/D converter. 05
- (B) Switched capacitor type DAC. 05

ALL THE BEST

KADI SARVA VISHWAVIDHYALAYA
BE 4th Semester Electronics & Communication Dept.
November-2014 Examination

Sub code: EC403

Date: 05/11/2014

Time: 10:30am to 01:30pm

Sub Name: Advanced Electronics

Total Marks: 70

Instructions:

1. Answer Each Section in Separate Answer sheet.
2. Use of Scientific Calculator is permitted. .
3. All questions are separate
4. Indicate clearly, the options you attempted along with its respective question number.
5. Use the last page of supplementary for rough work.

SECTION I

Q.1 (a)	Define following parameter. (1)CMMR (2) Fan-Out (3) Slew Rate (4) Propagation Delay (5) Power Dissipation.	[05]
(b)	Explain Tunnel diode with its negative resistance characteristics.	[05]
(c)	What is the negative feedback system? List the general characteristics of the negative feed back amplifier and explain any two of them with necessary equation.	[05]
OR		
(c)	Draw and Explain with necessary figure the single stage CE transistor Amplifier response.	[05]
Q.2 (a)	Explain Class B- Push Pull Amplifier	[05]
(b)	Explain Monostable operation of transistor amplifier.	[05]
OR		
Q.2 (a)	Explain Class B amplifier with its Cross over distortion.	[05]
(b)	Explain Class A power amplifier.	[05]
Q-3 (a)	Explain Block diagram of SMPS.	[05]
(b)	Write short note on Hybrid π model for a transistor on CE configuration and its circuit component.	[05]
OR		
Q-3 (a)	What is UJT? Explain UJT as relaxation oscillator.	[05]
(b)	Describe in detail: Series Voltage Regulator with overload protection.	[05]

SECTION II

Q.4 (a)	What is oscillator? Explain the concept of oscillation. Explain the concept of oscillation Properly with Barkhausen criteria.	[05]
(b)	What is Digital to Analog Convertor ? Draw and Explain Binary Weighted Resistor DAC ? Give the advantages and disadvantages of R-2R Digital to Analog convertor.	[05]
(c)	Give brief description of Crystal Oscillator.	[05]
	OR	
(c)	The 4% negative feedback is employed in an amplifier with $A_v=140$, $f_L=200\text{Hz}$ and $f_H=200\text{ kHz}$, $R_i=2\text{k}\Omega$, $R_o=4.7\text{k}\Omega$ Determine the following. A_{vf} , R_{if} , R_{of} , f_{LF} , f_{HF} .	[05]
Q.5 (a)	Explain working principal of colpitt's oscillator. Also derive the expression for frequency of oscillations.	[05]
(b)	Draw and explain Hartley oscillator using FET. Calculate the value of tank circuit capacitor of a hartley oscillator for 50 kHz with L_1 and L_2 are of 100 μH .	[05]
	OR	
Q.5 (a)	Draw the circuit and explain the operation of Wien bridge Oscillator and derive expression for feedback factor- β and frequency.	[05]
(b)	Design a colpitt oscillator to get frequency of 100 kHz with an active BJT having $h_{fe}=45$. Assume $C_1=0.001\text{ }\mu\text{f}$, $V_E=V_{ceq}=3\text{V}$, $I_{ceq}=1\text{mA}$.	[05]
Q-6 (a)	Explain working of successive approximation ADC with block diagram.	[05]
(b)	Explain Ideal Operational amplifier characteristics in detail.	[05]
	OR	
Q-6(a)	Draw 4-bit R-2R ladder type DAC and explain its working. Compare it with weighted resistor type DAC.	[05]
(b)	Explain ideal Op-Amp closed loop basic configuration.	[05]

KADI SARVA VISHWAVIDYALAYA

B.E SEMESTER : 4th

EXAMINATION (April - May / 2015)

SUBJECT CODE : EC - 403

SUBJECT NAME : Advance electronics

DATE: 02/05/2015

TIME: 10:30 am to 01:30 pm

TOTAL MARKS: 70

Instructions:

1. Answer each section in separate Answer Sheet.
2. Use of scientific Calculator is permitted.
3. All questions are compulsory.
4. Indicate **clearly**, the options you attempted along with its respective question number.
5. Use the last page of main supplementary for rough work.

Section - 1

Q:1 All Compulsory

- (A) Write and explain the types of amplifier base on its operation. Also find the efficiency of push pull amplifier. 05
- (B) Define: **1:** Harmonic Component. **2:** Valley Current for tunnel diode 05
3: Negative Resistance.
- (C) Write & Explain the principle of phase shift oscillator with its working. 05

OR

- (C) List out the Op-Amp Parameters. And explain any two in detail. 05
- Q:2 Answer the following Question.
- (A) Make short note on Hybrid π Capacitances for Transistor in detail. 05
- (B) Explain in brief UJT with its applications. 05

OR

- (A) Explain the operation of monostable multivibrator. 05
- (B) Design the binary Weighted Resistor Type DAC. 05
- Q:3 Answer the following Question.
- (A) What is Operational amplifier? Explain the Inverting and Non-inverting Amplifiers in detail. 10

OR

- (A) Derive the formula for negative feedback amplifier gain in term of A_f , A & β . 05
- (B) What do you understand by damped and undamped electrical oscillations? 05

Section - 2

Q:4 All Compulsory

- (A) Write and Explain Difference between positive feedback and negative feedback. 05
- (B) Quartz Crystal is commonly used in crystal Oscillations, why? 05

(C) Describe in detail: Dual Slope Type A/D Converter. 05

OR

(C) Draw & Explain over load protection circuit and Short circuit. 05

Q:5 Answer the following Question

(A) Draw and Explain the working of Hartley Oscillator also calculate the frequency of oscillation for a colpitts' oscillator in which feedback network consists of two capacitor of 100 pF & 20pF with 100mH coil across these two capacitors. 10

OR

(A) Make a short note on Voltage controlled switching circuits. 05

(B) Find the Single-Stage CE Transistor Amplifier Response. 05

Q:6 Answer the following Question

(A) Explain the power calculation of Class A amplifier and find its efficiency. Calculate the input power, output power & η of Class A amplifier when $V_{cc} = 20$, $R_b = 1K\Omega$, $R_c = 20\Omega$, $\beta = 25$ and base current of 10mA peak. 10

OR

(A) Make a Short note on Hybrid -pi CE Transistor Model. 05

(B) Make a Short note on Regulated Power Supply. 05

-----All the Best -----

Section - 2

KADI SARVA VISHWAVIDYALAYA

B.E SEMESTER : 4th

SUBJECT CODE : EC - 403

DATE: 27/10/2015

EXAMINATION (October / 2015)

SUBJECT NAME : Advance electronics

TIME: 10:30 am to 01:30 pm

TOTAL MARKS: 70

Instructions:

1. Answer each section in separate Answer Sheet.
2. Use of scientific Calculator is permitted.
3. All questions are compulsory.
4. Indicate **clearly**, the options you attempted along with its respective question number.
5. Use the last page of main supplementary for rough work.

Section - 1

Q:1 All Compulsory

- (A) Classify the amplifiers based on position of operation point (Q - Point) and also explain the Distortion in amplifier. 05
- (B) Write short note on mono stable multivibrator. 05
- (C) Explain the advantages and disadvantages of negative feedback. 05

OR

- (C) Explain construction and working of Tunnel diode. 05

Q:2 Answer the following Question.

- (A) Draw 4-bit R-2R ladder type DAC and explain its working. 05
- (B) Explain working of successive approximation ADC with block diagram. 05

OR

- (A) Draw the hybrid π model for a transistor in CE configurations and explain it. Derive the equation for transconductance gain. 05
- (B) Explain working principal of colpitt's oscillator. with necessary expression for frequency of Oscillations. 05

Q:3 Answer the following Question.

- (A) Determine the voltage gain, input and output impedance with feedback for voltage series feedback having 05

$$A = -100, R_i = 10 \text{ K}\Omega, R_o = 20 \text{ K}\Omega \text{ for feedback of}$$

a) $\beta = -0.1$ and

b) $\beta = -0.5$

- (B) Write short note on: Validity of Hybrid - PI model. 05

OR

- (A) Calculate, if $L = 800 \text{ mH}$, $C = 0.01 \text{ pF}$, $R = 1000 \Omega$ and $C_m = 20 \text{ pF}$ are the Various Value of an ac equivalent circuit of a piezoelectric crystal. Determine f_s and f_p of the crystal. 05
- (B) List out the Op-Amp Parameters. And explain any two in detail. 05

Section - 2

Q:4 All Compulsory

- (A) Define Oscillator. What are the requirement of positive feedback amplifier as an oscillator & also explain Barkhausen criterion of oscillations. 10
- (B) Derive the expression of voltage gain for inverting and non inverting mode of an OP-AMP. 05

OR

- (B) Design RC Phase shift oscillator for the Frequency of 10 KHz. 05

Q:5 Answer the following Question

- (A) Write and Explain Difference between positive feedback and negative feedback 05
- (B) Describe in detail: Voltage series regulator with the over load protection 05

OR

- (A) Explain in detail Push-Pull Amplifier. 05
- (B) Write down the limitation of RC and LC oscillators. Explain characteristic of crystal and base on that explain transistor crystal oscillator. 05

Q:6 Answer the following Question

- (A) Define the following parameter : 05
[1] Slew rate , [2] Fan Out, [3] Propagation Delay, [4] Harmonics Distortion, [5] Valley Current for tunnel diode
- (B) Explain the Switched mode power supply (SMPS) with necessary diagram. 05

OR

- (A) Explain UJT as a relaxation Oscillator 05
- (B) Draw and Explain Hartley oscillator using FET. Calculate the value of tank circuit capacitor of Hartley oscillator for 50 KHz with L1 and L2 are of 100 μ H. 05

-----All the Best -----