| Enrol. No.  |  |  |  |  |  |     |
|-------------|--|--|--|--|--|-----|
| Enion. 140. |  |  |  |  |  | No. |

## KADI SARVA VISHWAVIDHYALAYA

## LDRP INSTITUTE OF TECHNOLOGY & RESEARCH, GANDHINAGAR

## **B.E. Semester-IV**

## **MID-SEM EXAMINATION (FEB-2015)**

|      |       | te: 02/03/2015 Branch: Electrical Engineering Time: 12:00 to 1:30   |   |
|------|-------|---|---|
|      |       | bject Name: Digital Electronics   |   |
|      |       | x. Marks: 30  |   |
|      |       | tructions: All questions are compulsory   |   |
|      |       | igures to the <b>right</b> indicate full marks.   |   |
|      | 3) U  | Jse of scientific calculator is permitted   |   |
|      | 4) II | ndicate clearly, the options you attempt along with its respective question number.                         |   |
|      | 5) U  | Jse the last page of main supplementary for rough work  |   |
|      |       |   |   |
| Q.1. | (a)   | Reduced the following Boolean Expressions:  | 5 |
|      |       | $ ightharpoonup$ ABC[AB+ $\bar{C}$ (BC+AC)]   |   |
|      |       | $\rightarrow$ $(WX+W\overline{Y})(X+W)+WX(\overline{X}+\overline{Y})$                                       |   |
|      | (b)   | Do as Directed:   | 5 |
|      |       | $\triangleright$ (1101110.011) <sub>2</sub> = ( ) <sub>10</sub>   | J |
|      |       | $(2035)_8 = ()_{16}$  |   |
|      |       | $> (42FD)_{16} = ()_8$  |   |
|      |       | $(2056)_8 = (0.01)_{10}$  |   |
|      |       | $(A08F.EA)_{16} = ()_{10}$  |   |
| Q-2  | (a)   | Show that AB+ $(\overline{A+B})$ is equivalent to AOB with Truth Table and Logic diagrams.                  | 5 |
|      | (b)   | Explain De Morgan's Theorem with Truth Table and Logic Diagram.   | 5 |
|      |       | OR  |   |
|      | (a)   | Reduce the expression $\sum m(0,2,3,4,5,6)$ using mapping and implement it in AOI logic as well             | 5 |
| •    |       | as in NAND logic.   |   |
|      |       | as in the toget.  |   |
|      | (b)   | Reduce the expression $\sum m(0,1,2,3,5,7,8,9,10,12,13)$ using mapping and implement it in universal logic. | 5 |
|      |       |   |   |

Q-3(a) Do as Directed:

- $(10111.101)_2+(110111.01)_2$
- $> (173)_8 + (265)_8$
- > (A0FC)<sub>16</sub>+(B75F)<sub>16</sub>
- $\triangleright$  (5A9B)<sub>16</sub>×(7)<sub>16</sub>
- $\triangleright$  (462)<sub>8</sub>-(175)<sub>8</sub>
- (b) Prove that:


5

5

- ightharpoonup AB+A(B+C)+B(B+C)=B+AC
- $\rightarrow$   $(A+\bar{A})(AB+AB\bar{C}) = AB$

OR

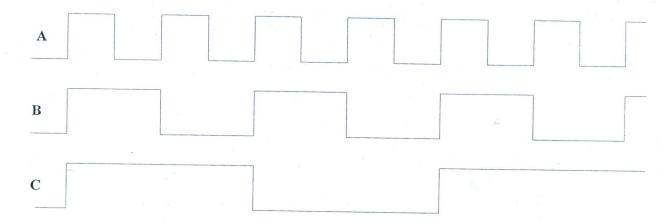Q-3(a) If the three waveforms A, B and C Shown in Fig. are applied to a three input AND gate, 5 determine the resulting output waveform.



(b) Write the Boolean expression for the logic diagram given below and simplify it as much as 5 possible and draw the logic diagram that implements the simplified expression.

